
 


# SECOND DERIVATIVE FILTER

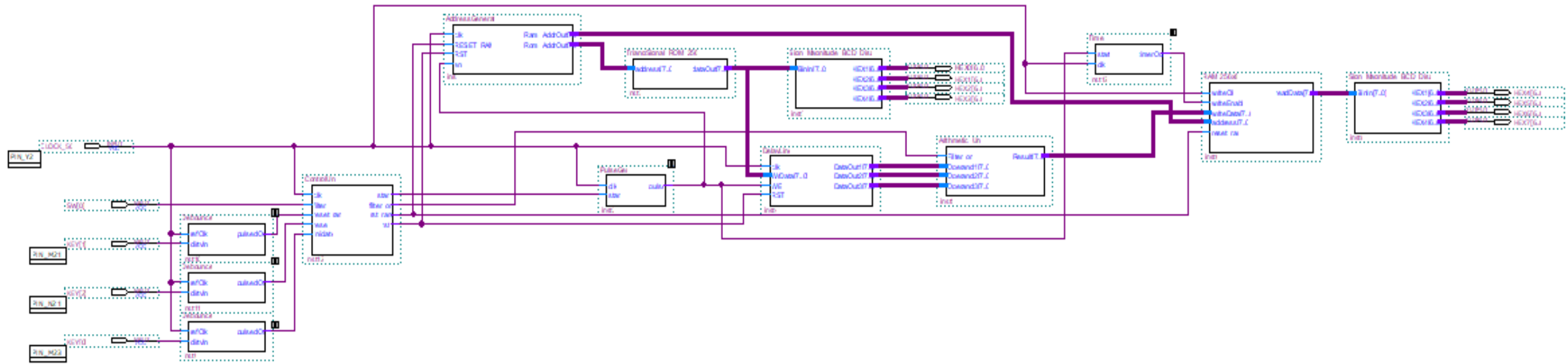

# CIRCUIT STRUCTURE [DIAGRAM]



# THE CIRCUIT HAS 13 PARTS

- 1 Pulse generator.
- 1 Address generator.
- 1 Rom.
- 1 Ram.
- 1 Delay line.
- 1 Timer.
- 3 Debouncers.
- 2 Binary converters for three 7 segment displays.

# CONTROL UNIT




## 5 INPUTS:

- **Clk** : Controlled by CLOCK\_50;
- **Filter** : Controlled by SW[0];
- **Reset\_ram** : Controlled by KEY[1]
- **Reset** : Controlled by KEY[2];
- **Iniciate** : Controlled by KEY[0];

## 4 OUTPUTS:

- **Start** : output that will start the count;
- **Filter\_on** : output that will start the filtering;
- **Rst\_ram** : output that will clean the RAM and stop the count;
- **Rst** : output that resets the whole circuit;


# DEBOUNCER

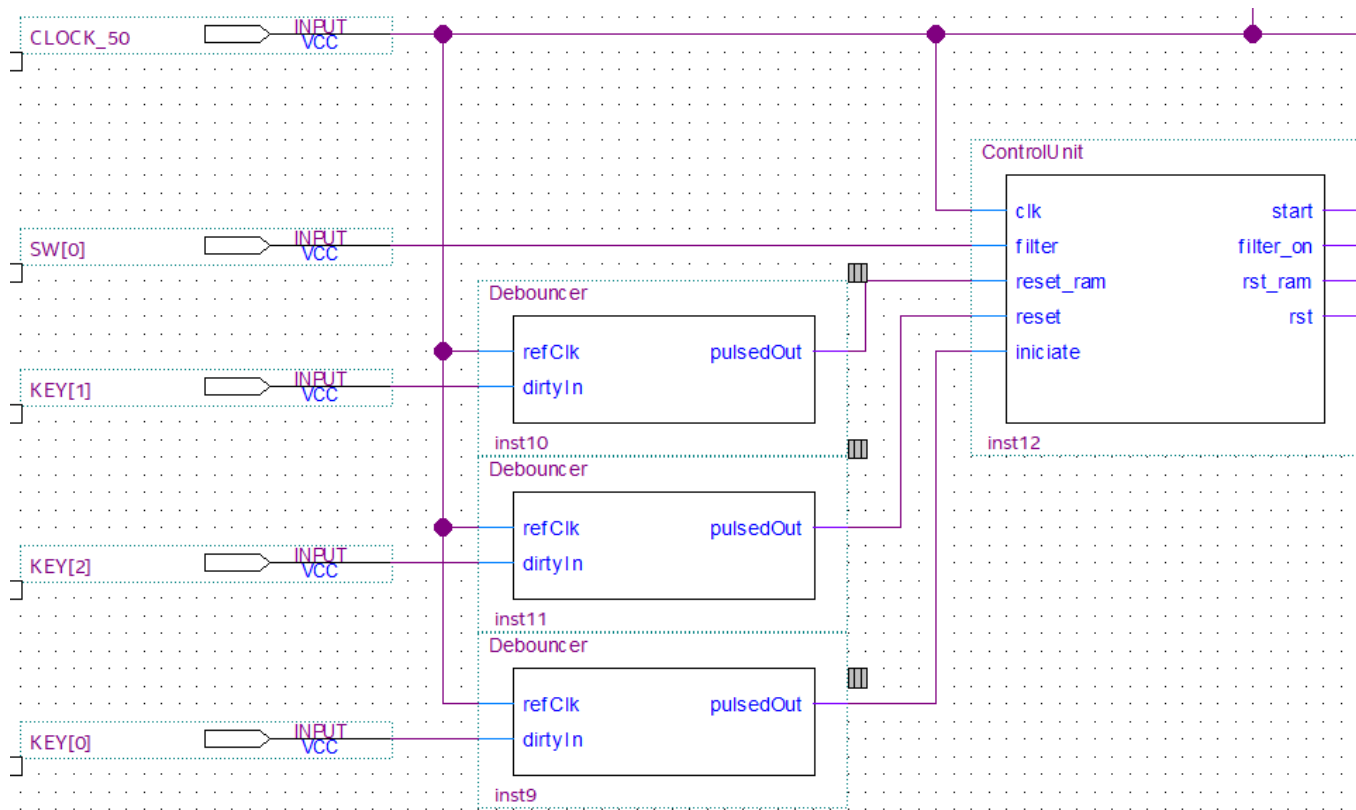

Three DEBOUNCERES are needed!

- 1 for KEY[0];
- 1 for KEY[1];
- 1 for KEY[2];

# PULSE GENERATOR

 


## 2 INPUTS:

- **Clk** : Controlled by CLOCK\_50;
- **Start** : Controlled by the initiation of the CONTROL UNIT;

## 1 OUTPUT:

- **Pulse** : Generated Pulse every 0.5 seconds;

# ADDRESS GENERATOR

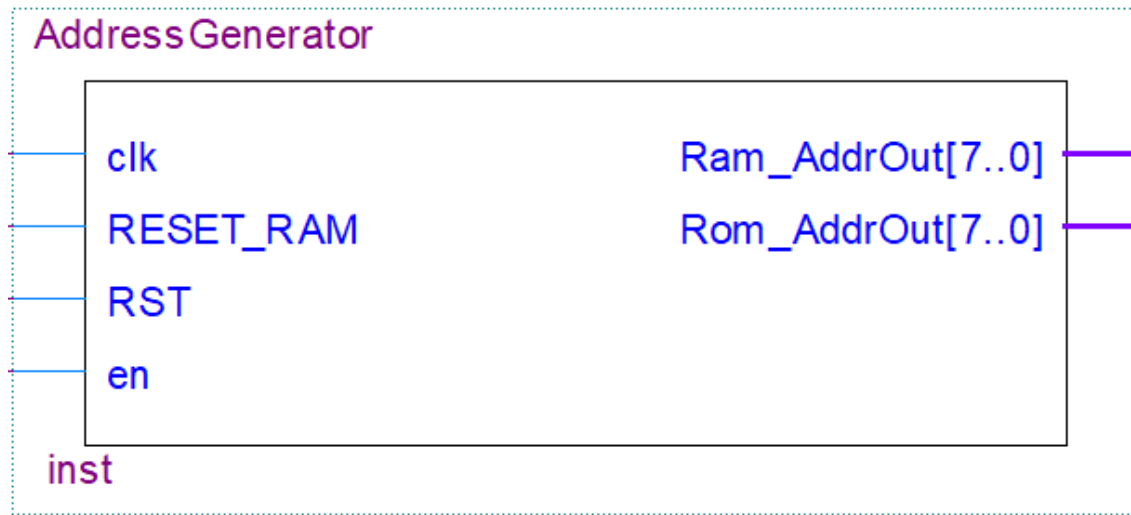

## 4 INPUTS:

- **Clk** : Controlled by CLOCK\_50;
- **RESET\_RAM** : Controlled by rst\_ram from CONTROL UNIT;
- **RST** : Controlled by rst from CONTROL UNIT;
- **En** : Controlled by the pulse from PULSE GENERATOR;


## 2 OUTPUTS:

- **Ram\_AddrOut** : RAM address;
- **Rom\_AddrOut** : ROM address;

# CAN BE DEVIDED INTO 2 PARTS!


## 1) Rom address generator:

- Only has a global reset.

 

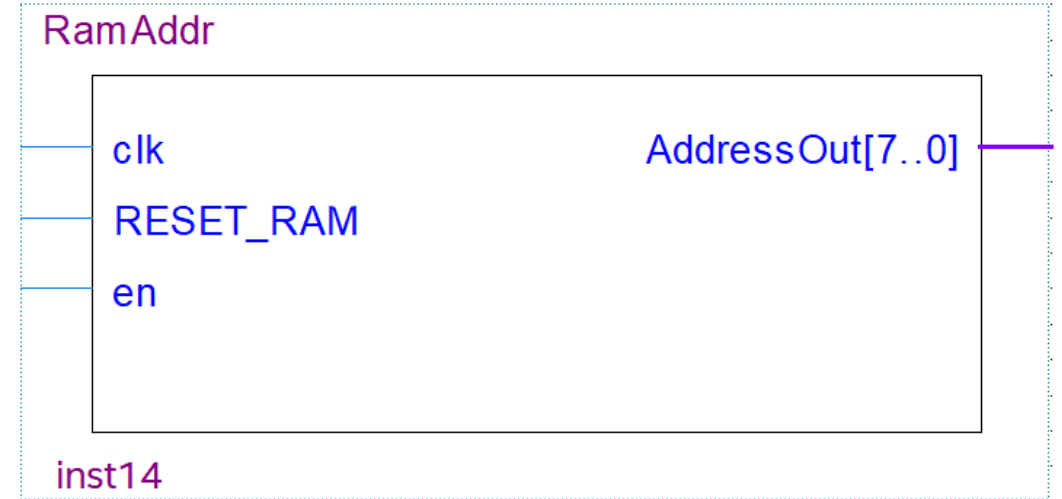
## 2) Ram address generator:

- Has both a global reset and a ram only reset.





# 256X8 ROM

 


## 1 INPUT:

- **Address** : Controlled by ADDRESS GENERATOR;

## 1 OUTPUT:

- **DataOut** : Value from ROM for each address (predefined);

# DELAY LINE

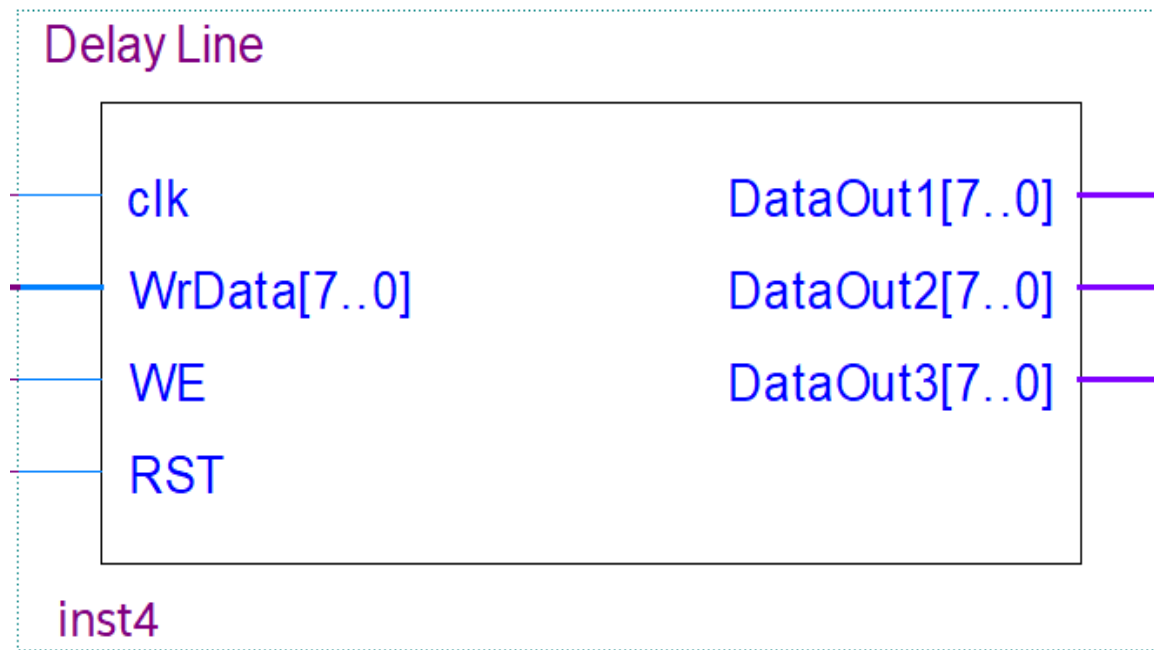


## 4 INPUTS:

- **Clk** : Controlled by CLOCK\_50;
- **WrData** : ROM values;
- **WE** : Activated by the PULSE GENERATOR;
- **RST** : Global reset, controlled by CONTROL UNIT

## 3 OUTPUTS:

- **DataOut1** : "k+1" value;
- **DataOut2** : "k" value;
- **DataOut3** : "k-1" value;

# ARITHMETIC UNIT

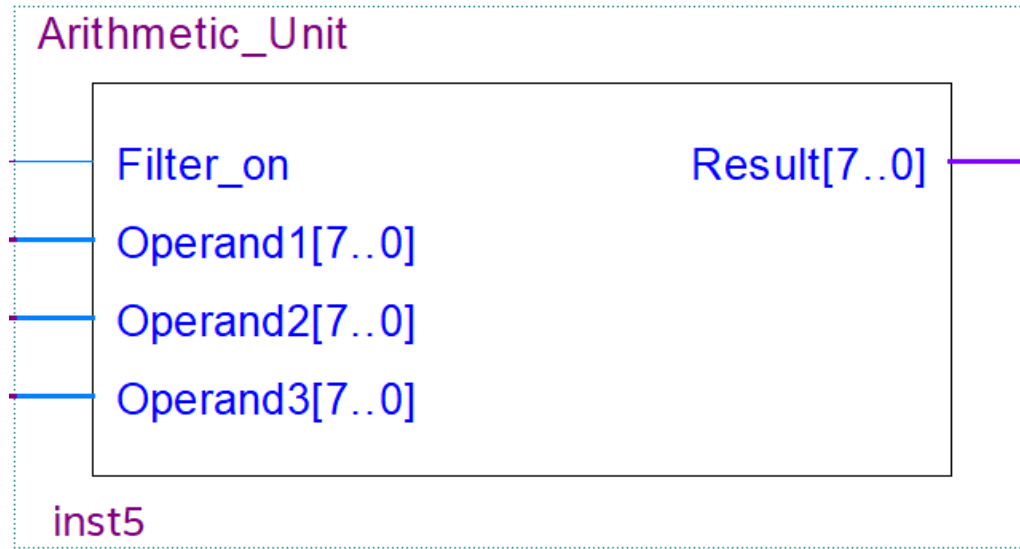

## Filter operation

$$y_k = x_{k+1} - 2x_k + x_{k-1} \quad k = 1, \dots, 254,$$
$$y_0 = x_0, y_{255} = x_{255}$$


### 4 INPUTS:

- **Filter\_on** : Controlled by CONTROL UNIT;
- **Operand1** : "K+1" from DELAY LINE;
- **Operand2** : "K" from DELAY LINE;
- **Operand3** : "K-1" from DELAY LINE;

### 1 OUTPUT:

- **Result** : Filter operation result.

# 256X8 RAM

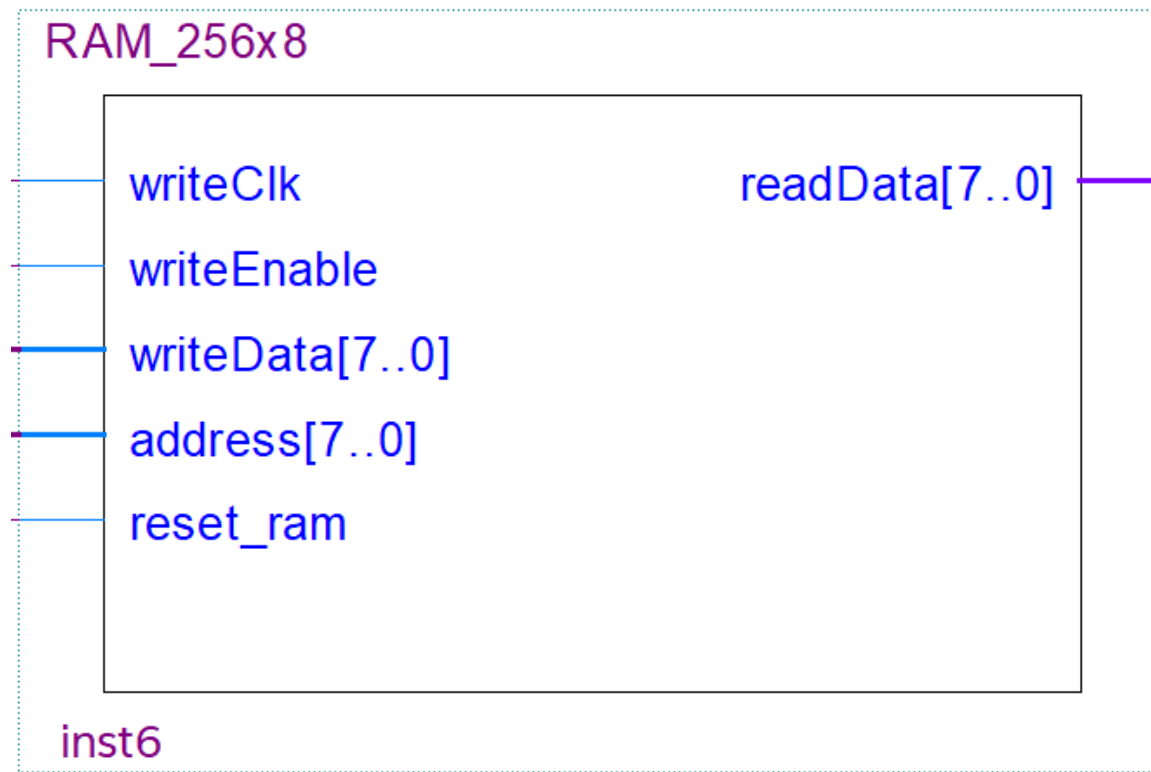


## 5 INPUTS:

- **WriteClk** : Controlled by CLOCK 50;
- **WriteEnable** : Activated by TIMER;
- **WriteData** : Result from ARITHMETIC UNIT;
- **Address** : Controlled by ADDRESS GENERATOR;
- **Reset\_ram** : Controlled by rst\_ram from CONTROL UNIT;

## 1 OUTPUT:

- **ReadData** : Value of RAM in the current address;

# TIMER

 


## 2 INPUTS:

- **Clk** : Controlled by CLOCK\_50;
- **Start** : Activated by the pulse from PULSE GENERATOR;

## 1 OUTPUT:

- **TimerOut** : Output sent after the count;

# SIGN MAGNITUDE BCD DISPLAY

 

## 1 INPUTS:


- **BinIn** : Binary value to be displayed;

## 4 OUTPUT:


- **HEX1** : Value sent to the first display;
- **HEX2** : Value sent to the second display;
- **HEX3** : Value sent to the third display;
- **HEX4** : Value sent to the fourth display;

# CAN ALSO BE DIVIDED INTO 2 PARTS!

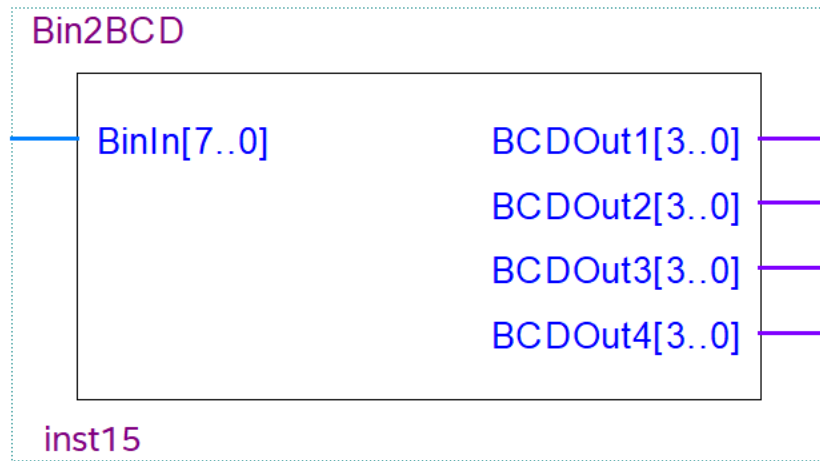1) 8 bit binary number to 4 BCD numbers of 4 bits each converter.



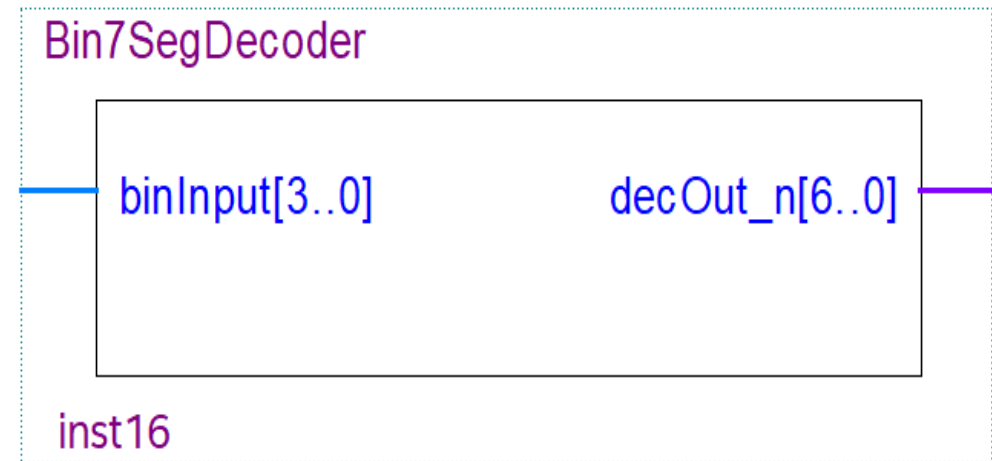2) 4 bit BCD number to 7 segment display converter.



PUTTING EVERY PIECE TOGETHER...

## 4 INPUTS:

- KEY[0] : Start;
- KEY[1] : Reset Ram;
- KEY[2] : Reset;
- SW[0] : Filter On;

## 8 OUTPUTS:

- HEX0 to HEX3: ROM values;
- HEX4 to HEX7: RAM values;

**And the following circuit:**

